

8. What is the material used for hydraulic tubing that  
to intense heat?
- 

9. What type of line is used to connect moving parts?
-

**CNTT-M1702**

PREPARED BY

NAVAL AIR TECHNICAL TRAINING CENTER  
NAVAL AIR STATION MEMPHIS  
MILLINGTON TENNESSEE

PREPARED FOR  
CHIEF OF NAVAL TECHNICAL TRAINING

NOVEMBER 1984

第一、二、三、四、五、六、七、八、九、十、十一、十二、十三、十四、十五、十六、十七、十八、十九、二十、二十一、二十二、二十三、二十四、二十五、二十六、二十七、二十八、二十九、三十、三十一、三十二、三十三、三十四、三十五、三十六、三十七、三十八、三十九、四十、四十一、四十二、四十三、四十四、四十五、四十六、四十七、四十八、四十九、五十、五十一、五十二、五十三、五十四、五十五、五十六、五十七、五十八、五十九、六十、六十一、六十二、六十三、六十四、六十五、六十六、六十七、六十八、六十九、七十、七十一、七十二、七十三、七十四、七十五、七十六、七十七、七十八、七十九、八十、八十一、八十二、八十三、八十四、八十五、八十六、八十七、八十八、八十九、九十、九十一、九十二、九十三、九十四、九十五、九十六、九十七、九十八、九十九、一百。





and on you being safety conscious at all times. It is the responsibility of all Navy and Marine Corps personnel to prevent accidents. This can be done if everyone develops and practices conscientious safety habits and observes all precautions when performing maintenance of any type. Always remember:

SAFETY CANNOT BE OVERSTRESSED!!!!

the Advanced First-Term Avionics Course (Class A1). Amplification has been provided for all homework assignments and any additional notes you may desire. Remember that all homework is MANDATORY.

Book contains the following:

Assignments necessary to accomplish the Unit II objectives.

LUCK!!!!

The schedule is as follows:

| TOPIC NO.   | TYPE  | PERIOD                           |                      |
|-------------|-------|----------------------------------|----------------------|
| SECOND WEEK |       |                                  |                      |
| Fifth Day   |       |                                  |                      |
| 2.1         | Class | 77<br>78<br>79                   | Series R             |
| 2.2         | Class | 80                               | Parallel             |
| THIRD WEEK  |       |                                  |                      |
| First Day   |       |                                  |                      |
| 2.2         | Class | 81                               | Parallel             |
| 2.3         | Class | 82<br>83<br>84                   | Physics              |
| 2.4         | Class | 85<br>86<br>87<br>88             | Semicond<br>Physics  |
| Second Day  |       |                                  |                      |
|             | Class | 89                               | Semicond<br>Physics  |
|             | Lab   | 90                               | PN Junct<br>(Laborat |
|             | Class | 91<br>92<br>93<br>94<br>95<br>96 | Junction<br>tors     |

|             |       |     |                                             |
|-------------|-------|-----|---------------------------------------------|
|             |       | 98  |                                             |
|             |       | 99  |                                             |
|             |       | 100 |                                             |
| 2.8         | Class | 101 | Biasing A<br>ments                          |
|             |       | 102 |                                             |
|             |       | 103 |                                             |
|             |       | 104 |                                             |
| Fourth Day  |       |     |                                             |
| 2.8         | Class | 105 | Biasing A<br>ments                          |
|             |       | 106 |                                             |
|             |       | 107 |                                             |
| 2.9         | Lab   | 108 | Biasing A<br>ments (Lab                     |
|             |       | 109 |                                             |
|             |       | 110 |                                             |
|             |       | 111 |                                             |
|             |       | 112 |                                             |
| Fifth Day   |       |     |                                             |
|             | Class | 113 | Unit/Modu<br>Criterion<br>Written E<br>tion |
|             |       | 114 |                                             |
|             |       | 115 |                                             |
| 2.10        | Class | 116 | Decibels                                    |
|             |       | 117 |                                             |
| 2.11        | Class | 118 | Feedback<br>Amplifier                       |
|             |       | 119 |                                             |
|             |       | 120 |                                             |
| Fourth Week |       |     |                                             |
| First Day   |       |     |                                             |
| 2.11        | Class | 121 | Feedback<br>Amplifier                       |
|             |       | 122 |                                             |



|            |       |     |      |
|------------|-------|-----|------|
|            |       | 125 | Ampl |
|            |       | 126 |      |
|            |       | 127 |      |
|            |       | 128 |      |
| Second Day |       |     |      |
| 2.13       | Class | 129 | Tra  |
|            |       |     | Cou  |
|            |       | 130 |      |
|            |       | 131 |      |
| 2.14       | Class | 132 | Spe  |
|            |       | 133 |      |
|            |       | 134 |      |
|            |       | 135 |      |
|            |       | 136 |      |
| Third Day  |       |     |      |
| 2.14       | Class | 137 | Spe  |
|            |       | 138 |      |
|            |       | 139 |      |
| 2.15       | Class | 140 |      |
|            |       | 141 | Vac  |
|            |       |     | Fur  |
| 2.16       | Class | 142 |      |
|            |       | 143 | Tri  |
|            |       | 144 |      |
| Fourth Day |       |     |      |
| 2.16       | Class | 145 | Tri  |
|            |       | 146 |      |
|            |       | 147 |      |
| 2.17       | Class | 148 |      |
|            |       | 149 | Mul  |
|            |       | 150 |      |
|            |       | 151 |      |
|            |       | 152 |      |

154

155

156

day when the lesson was completed. Each assignment sheet is checked by an instructor for corrections and completion. Information sheets assigned with lesson topics are considered homework. Failure to complete assigned homework may result in disciplinary action.

Assignment Sheet

Period

2.1.1A

2.2.1A

2.3.1A

2.4.1A

2.6.1A

2.8.1A

2.10.1A

2.11.1A

2.12.1A

2.13.1A

2.14.1A

2.15.1A

2.16.1A

2.17.1A

## UNIT LEARNING OBJECTIVES

### TERMINAL OBJECTIVES

- 1.0 SOLVE problems related to electronic circuits, using mathematics, algebra, and trigonometry. A formula, trigonometric tables, and a universal Time Constant will be provided. Performance must be in accordance with mathematical principles outlined in "Mathematics," NAVPERS 10069-series, "Mathematics," Vol. III, NAVPERS 10073-series, "Basic Electronics," Vol. I, NAVPERS 10087-series, and "Basic Electricity," NAVPERS 10086-series. Performance will be measured by a written multiple-choice examination.
- 2.0 ANALYZE the internal structure and operation of semiconductor junctions by tracing majority and minority current flow through a given semiconductor device in accordance with quantum mechanical principles outlined in "Basic Electronics," Vol. I, NAVPERS 10087-series, and "Aviation Electronics Technician 3 & 2," NAVEDTRA 10087-series. Performance will be measured by a written multiple-choice examination.
- 3.0 Mathematically ANALYZE the operation of given semiconductor circuits by solving problems in terms of current, reactance, and frequency. A formula sheet will be provided. Responses must be in accordance with "Basic Electronics," Vol. I, NAVPERS 10087-series, and "Basic Electricity," Vol. I, NAVPERS 10086-series. Performance will be measured by a written multiple-choice examination.
- 4.0 ANALYZE the internal structure and operation of semiconductor circuits by identifying elements and their functions, solving problems in terms of voltage, current resistance, and biasing. Responses must be in accordance with information outlined in "Basic Electronics," Vol. I, NAVPERS 10087-series. Performance will be measured by a written multiple-choice examination. A formula sheet will be provided.

### ENABLING OBJECTIVES

- 1.1 SOLVE problems involving addition, subtraction, multiplication, and division of radicals and exponents, using the laws of exponents. Response must be in accordance with "Mathematics," Vol. I, NAVPERS 10069-series. Performance will be measured by a written multiple-choice examination.

A formula sheet will be provided.

- 1.3 SOLVE for the variables in simultaneous linear equations using the principles of matrix algebra. Responses in accordance with "Mathematics," Vol. III, NAVPERS 10086-series. Performance will be measured by a written multiple-choice examination. A formula sheet will be provided.
- 1.4 SOLVE for total capacitance, RC time, current, and values of a simple RC switching circuit. Response in accordance with "Basic Electricity," NAVPERS 10086-series. Performance will be measured by a written multiple-choice examination. A formula sheet and a Universal Time Constant chart will be provided.
- 1.5 SOLVE for total inductance, L/R time, current, and values of a simple L/R switching circuit. Response in accordance with "Basic Electricity," NAVPERS 10086-series. Performance will be measured by a written multiple-choice examination. A formula sheet and a Universal Time Constant Chart will be provided.
- 1.6 SOLVE for unknown current, voltage, and resistance of electronic circuits containing source characteristics and voltage dividers. Response must be in accordance with "Basic Electricity," NAVPERS 10086-series. Performance will be measured by a written multiple-choice examination. A formula sheet will be provided.
- 1.7 SOLVE for unknown values of current, voltage, reactance, and power in series and parallel a-c circuits. Response must be in accordance with "Basic Electricity," NAVPERS 10086-series. Performance will be measured by a written multiple-choice examination. A formula sheet and trigonometric tables will be provided.
- 1.8 SOLVE for unknown values of current, voltage, reactance, frequency, bandwidth,  $m$  and circuit "Q", in series and parallel resonant circuits. Response will be in accordance with "Basic Electronics," Vol. I, NAVPERS 10087-series. Performance will be measured by a written multiple-choice examination. A formula sheet and trigonometric tables will be provided.

series. Performance will be measured by a written multiple-choice examination.

SELECT, from given lists, correct statements related to properties of heat, sound, cryogenics, and the electromagnetic spectrum. Responses must be in accordance with "Aviation Electronics Technician 3 & 2," NAVEDTRA 1031-series. Performance will be measured by a written multiple-choice examination.

DETERMINE normal biasing polarities of semiconductor junctions by ANALYZING majority and minority current through a given semiconductor circuit. Responses must be in accordance with quantum principles outlined in "Basic Electronics," Vol. I, NAVPERS 10087-series. Performance will be measured by a written multiple-choice examination.

DETERMINE biasing arrangements of semiconductor circuit by SOLVING problems in terms of voltage, current, reactance, and frequency. Responses must be in accordance with "Basic Electronics," Vol. I, NAVPERS 10087-series. Performance will be measured by a written multiple-choice examination. A formula sheet will be provided.

DETERMINE capabilities, electrical characteristics, advantages and disadvantages of given semiconductor circuits by SOLVING problems in terms of voltage, current, reactance, and frequency. Responses must be in accordance with "Basic Electronics," Vol. I, NAVPERS 10087-series. A formula sheet will be provided.

COMPUTE decibel gain and loss in terms of the voltage power of a given semiconductor amplifier circuit. Responses must be in accordance with "Basic Electronics," Vol. I, NAVPERS 10087-series. A formula sheet will be provided. Performance will be measured by a multiple-choice examination.

BUILD basic semiconductor amplifier circuits (under supervision). MEASURE values and RECORD measurements, calculations, and evaluations on a job sheet, given necessary equipment and an RCA 6F16 transistor trainer. Accuracy will be measured in accordance with information contained in "Basic Electronics," Vol. I, NAVPERS 10087-series.

SOLVE problems in terms of voltage, current, resistance, biasing, using vacuum-tube formulas and tube constants. Responses must be in accordance with information outlined in "Basic Electronics," Vol. I, NAVPERS 10087-series. Performance will be measured by a written multiple-choice examination. A formula sheet will be provided.

|                                          |  |
|------------------------------------------|--|
| Foreword . . . . .                       |  |
| Safety Notice. . . . .                   |  |
| How to Use This Assignment Book. . . . . |  |
| Unit II Class Schedule . . . . .         |  |
| Unit II Homework Schedule. . . . .       |  |
| Unit Learning Objectives . . . . .       |  |

## Assignments

|                                    |  |
|------------------------------------|--|
| Assignment Sheet 2.1.1A. . . . .   |  |
| Assignment Sheet 2.2.1A. . . . .   |  |
| Assignment Sheet 2.3.1A. . . . .   |  |
| Assignment Sheet 2.4.1A. . . . .   |  |
| Assignment Sheet 2.6.1A. . . . .   |  |
| Assignment Sheet 2.8.1A. . . . .   |  |
| Assignment Sheet 2.10.1A . . . . . |  |
| Assignment Sheet 2.11.1A . . . . . |  |
| Assignment Sheet 2.12.1A . . . . . |  |
| Assignment Sheet 2.13.1A . . . . . |  |
| Assignment Sheet 2.14.1A . . . . . |  |
| Assignment Sheet 2.15.1A . . . . . |  |
| Assignment Sheet 2.16.1A . . . . . |  |
| Assignment Sheet 2.17.1A . . . . . |  |

## Formula Sheet






The purpose of this assignment sheet is to familiarize you with various aspects of series resonant circuits. Consideration is given to both an operational analysis and mathematical analysis, as well as certain characteristics unique to these circuits.

#### LESSON TOPIC LEARNING OBJECTIVES

- 1.8.1. SELECT, from a list of circuit conditions, those that apply to a series resonant circuit.
- 1.8.2. SOLVE, given a series circuit with specified values of inductance and capacitance, for the resonant frequency.
- 1.8.3. SOLVE, given a series resonant circuit with specified values of capacitance and the resonant frequency, for the value of inductance.
- 1.8.4. SOLVE, given a series resonant circuit with specified values of inductance and the resonant frequency, for the value of capacitance.
- 1.8.5. SOLVE, given a series resonant circuit with specified values of  $X_L$ ,  $X_C$ ,  $R$  and  $F_0$ , for the series resonant functions of  $Q$ ,  $BW$ ,  $f_1$ ,  $f_2$ .
- 1.8.6. SOLVE, given a series resonant circuit with specified values of  $X_L$ ,  $X_C$ ,  $R$  and  $E_a$ , for  $E_C$ ,  $E_L$ , and  $E_R$ .
- 1.8.7. SELECT, from a list provided, circuit characteristics above and below resonance.
- 1.8.8. IDENTIFY and LABEL frequency response curves to include:
  - a. An impedance response curve of a series circuit.
  - b. A current response curve of a series resonant circuit.
  - c.  $Z_{min}$ ,  $I_{max}$ ,  $I_{f1}$ ,  $I_{f2}$ ,  $Z_{f2}$ .
- 1.8.9. SOLVE, for series resonant circuit functions,  $P_a$ ,  $P_f$ , using specified values of current, voltage, and resistance.

1. Circle the letter beside each condition listed below that applies to a series resonant circuit.
- |                                  |                    |
|----------------------------------|--------------------|
| a. $Z$ is minimum                | g. $I$ is maximum  |
| b. $P_t$ is greater than $P_a$ . | h. Phase Angle is  |
| c. $X_L = X_C$                   | i. $Z = R$         |
| d. $I$ is minimum.               | j. $Z$ is maximum. |
| e. P. F. = 1                     | k. $P_t = P_a$     |
| f. Phase angle = $0^\circ$ .     |                    |
2. What is the resonant frequency of the circuit below

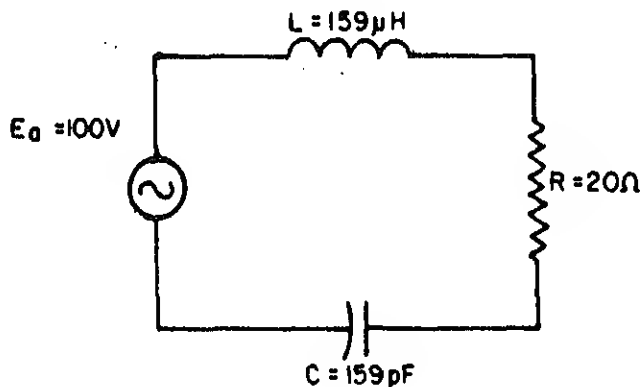

$f_o =$  \_\_\_\_\_

L = \_\_\_\_\_

What value of capacitance must be used with a .318 H coil have a series circuit resonant to 95 kHz?

C = \_\_\_\_\_

following results in a series resonant circuit.


Results

App  
fre

$X_L$  becomes  $X_Y$

Circuit appears capacitive and resistive to the source.

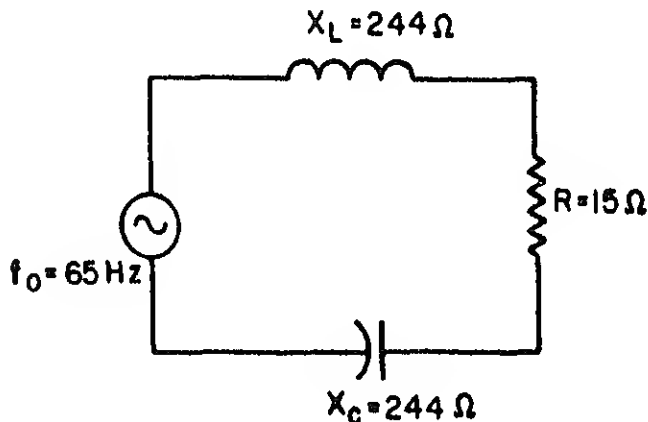6. Using the circuit values below, solve for  $Q$ , BW,  $f_1$ ,  $f_2$ .



$Q =$


BW =

$f_1 =$


$f_2 =$

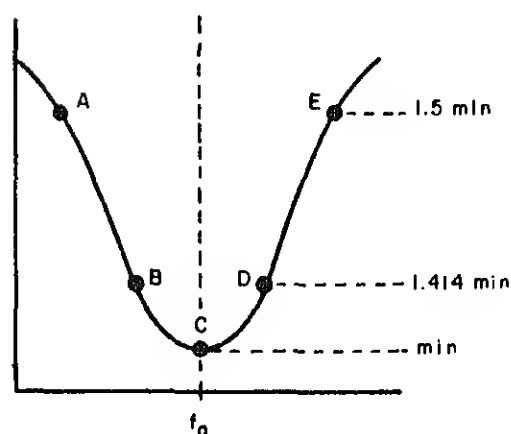7. A series resonant circuit that has a high L to C ratio is a \_\_\_\_\_ circuit  $Q$  and a \_\_\_\_\_ bandwidth.

- Label the impedance response curve of a series resonant circuit.
- Label the current response curve of a series resonant circuit.
- Fill in each blank with the letter which represents the corresponding point on the proper graph.




\_\_\_\_\_  
(type)

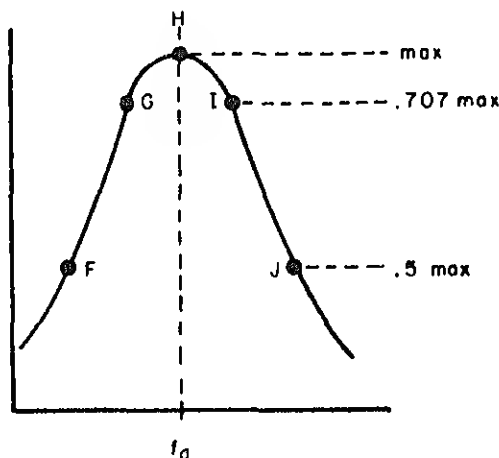

\_\_\_\_\_  
(type)

|         |                 |                 |
|---------|-----------------|-----------------|
| x _____ | $Z_{f_1}$ _____ | $I_{f_1}$ _____ |
| n _____ | $Z_{f_2}$ _____ | $I_{f_2}$ _____ |

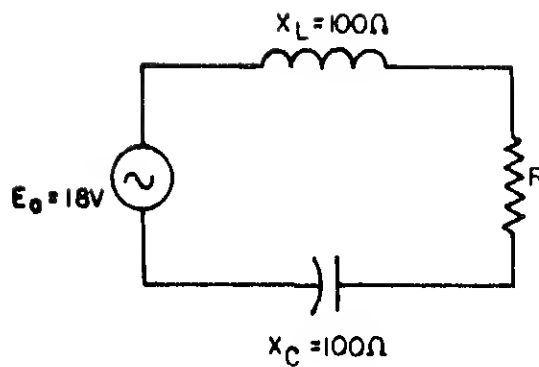


$$P_a = \underline{\hspace{2cm}}$$

$$P_t = \underline{\hspace{2cm}}$$

$$P_f = \underline{\hspace{2cm}}$$

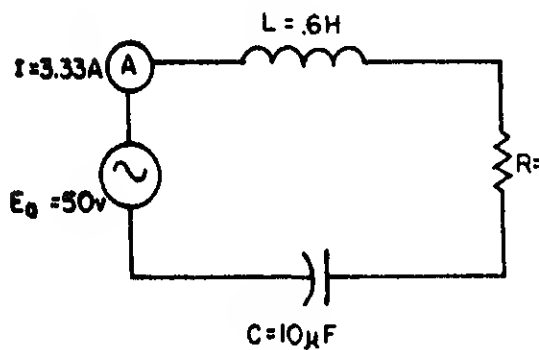10. Using the series resonant circuit values shown below, solve for  $E_C$ , and  $E_R$ .



$$E_L = \underline{\hspace{2cm}}$$

$$E_C = \underline{\hspace{2cm}}$$

$$E_R = \underline{\hspace{2cm}}$$

## INTRODUCTION

The purpose of this assignment sheet is to familiarize you with various aspects of parallel resonant circuits. Considerations will be given to both an operational analysis and mathematical analysis as well as certain characteristics unique to these circuits.


### LESSON TOPIC LEARNING OBJECTIVES

- 1.8.10. SELECT, from a list provided, the correct function for  $I_{line}$  in a parallel resonant circuit.
- 1.8.11. SELECT, from a list provided, the condition of  $I_{line}$  in a parallel circuit at resonance.
- 1.8.12. SOLVE, given specified values of  $L$  and  $C$ , for the resonant frequency.
- 1.8.13. SOLVE, given the values of  $R$ ,  $X_C$ ,  $X_L$ , and  $E_a$ , for the correct values of  $Q$ ,  $Z$ ,  $I_{line}$ , and  $I_{circ}$ .
- 1.8.14. SELECT, from a given list, the correct purpose of a swamping resistor in a parallel resonant circuit.
- 1.8.15. SELECT, from a list provided, circuit characteristics above and below resonance.
- 1.8.16. IDENTIFY and LABEL the following on given frequency response curves:
  - a. The impedance response curve of a parallel resonant circuit.
  - b. The current response curve of a parallel resonant circuit.
  - c. The following points indicated on the curves:
    - (1)  $Z_{max}$
    - (2)  $I_{min}$
    - (3)  $I_{f1}$  and  $I_{f2}$
    - (4)  $Z_{f1}$  and  $Z_{f2}$
- 1.8.17. SOLVE, for the parallel resonant circuit function  $P_{avg}$  and  $P_f$  using specified values of  $E_{app}$  and  $I_{line}$ .




2. When a parallel circuit is operating at its resonant frequency,  $I_{\text{circ}}$  is \_\_\_\_\_ and  $I_{\text{line}}$  is \_\_\_\_\_  
(minimum/maximum)
- \_\_\_\_\_ (minimum/maximum)

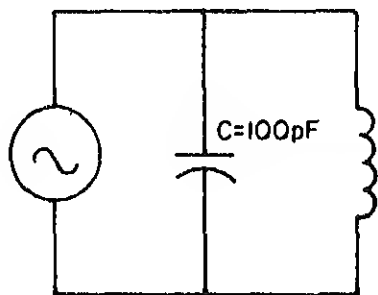3. Solve for the resonant frequency of the circuit below.



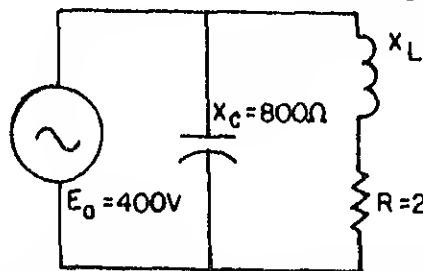4. Using circuit values shown below, solve for the following:  $Q$ ,  $Z$ ,  $I_{\text{line}}$ ,  $I_{\text{circ}}$ .



5. Solve for the bandwidth of a parallel resonant circuit, using the following information:  $F_0 = 1500$  kHz,  $X_L = 2400 \angle +90^\circ$  ohms,  $R = 8 \angle 0^\circ$  ohms.

What is the characteristic impedance of a parallel circuit

- a. at the resonant frequency? \_\_\_\_\_
- b. below the resonant frequency? \_\_\_\_\_
- c. above the resonant frequency? \_\_\_\_\_



the purpose of this assignment sheet is to familiarize you with the material covered in the physics overview lesson.

## LESSON TOPIC LEARNING OBJECTIVES

- 2.2.1. SELECT, from a list provided, the three forms in which matter can exist.
- 2.2.2. SELECT, from a list provided, the definition of mass.
- 2.2.3. SELECT, from a list provided, the definition of volume.
- 2.2.4. SELECT, from a list provided, the definition of density.
- 2.2.5. SELECT, from a list provided, the definition of temperature.
- 2.2.6. SELECT, from a list provided, the relationship between energy and matter.
- 2.2.7. SELECT, from a list provided, the definition of heat.
- 2.2.8. SELECT, from a list provided, the definition of conductivity.
- 2.2.9. SELECT, from a given list, the definition of sound.
- 2.2.10. SELECT, from a given list, the definition of frequency.
- 2.2.11. SELECT, from a given list, the definition of the electromagnetic spectrum.
- 2.2.12. SELECT, from a given list, the definition of heat transfer.
- 2.2.13. SELECT, from a given list, the definition of temperature.
- 2.2.14. SELECT, from a given list, the six sources of heat.
- 2.2.15. MATCH, given a list of definitions, the terms British Thermal Unit, calorie, and Calorie.
- 2.2.16. MATCH, given a list of definitions, the terms conduction, convection, and radiation with their respective definitions.

2. State the definition of cohesion.
3. Define mass.
4. State Newton's Law of Inertia.
5. State the definition of adhesion.
6. Give the definition of energy.
7. List the two kinds of energy.
8. State the relationship between matter and energy.
9. State the definition of cryogenics.
10. Give the definition of absolute zero.
11. Give the definition of superconductivity.
12. What is the velocity of sound at sea level at 30°C?
13. Give the frequency range of the audio spectrum.
14. Define light.
15. Give the definition of the optical spectrum.
16. Define heat.

- b. Temperature is a measure of the ability of a material to contain heat.
- c. Temperature is a measure of the absorption or release of heat by a material over a period of time.
- d. Temperature is a measure of the ability of a material to generate heat from contact with another material.

18. List the six sources of heat.

1. \_\_\_\_\_ 2. \_\_\_\_\_ 3. \_\_\_\_\_ 4. \_\_\_\_\_
5. \_\_\_\_\_ 6. \_\_\_\_\_

19. Match the units of heat measurement in column A with definitions in column B.

A

B

\_\_\_\_ (1) One B.T.U.

\_\_\_\_ (2) One Calorie

\_\_\_\_ (3) One Calorie

a. The quantity of heat needed to raise the temperature of one Kilogram of water one Celsius (centigrade) degree.

b. The quantity of heat needed to raise the temperature of one Kilogram of water one Fahrenheit degree.

c. The quantity of heat needed to raise the temperature of one gram of water one Celsius (centigrade) degree.

d. The quantity of heat needed to raise the temperature of one gram of water one Fahrenheit degree.

20. Match each term in column A with its definition in

\_\_\_\_(1) Conduction

a. Transfer of heat by electron flow

\_\_\_\_(2) Convection

b. Transfer of heat by motion of a fluid

\_\_\_\_(3) Radiation

c. Transfer of heat by molecule to molecule

d. Transfer of heat by electromagnetic waves

e. Transfer of heat by mechanical means

The purpose of this assignment sheet is to familiarize you with various aspects of semiconductor physics and PN junctions. Consideration will be given to the operational analysis and characteristics of the unique characteristics of semiconductor devices.

## LESSON TOPIC LEARNING OBJECTIVES

- 2.1.1 MATCH, given a list, the terms molecule, element, atom, with their respective definitions.
- 2.1.2 NAME, given a diagram, three sub-atomic particles in an atom.
- 2.1.3 STATE the requirements for chemical stability of an atom.
- 2.1.4 CALCULATE, given the correct formula, the maximum number of electrons in a specified energy shell of an atom.
- 2.1.5 SELECT, given a list, the three types of bonding that occurs between atoms.
- 2.1.6 MATCH, given a list of definitions, the terms conductor, semiconductor, and insulator with their respective definitions.
- 2.1.7 SELECT, from a given list, the requirements for moving a valence electron into mobility.
- 2.1.8 SELECT, from a given list, the definition of covalent bonding.
- 2.1.9 SELECT, from a given list, the number of valence electrons in donor and acceptor atoms.
- 2.1.10 STATE, in the space provided, which type of impurity will produce N- or P- type materials, when added to silicon or germanium.



- 2.3.3 SELECT, from a given list, the definition of
- 2.3.4 SELECT, from a given list, why ions are present at the junction of an unbiased PN junctions.
- 2.3.5 DRAW, in the space provided, a PN junction, showing the potential barrier with its proper polarities.
- 2.3.6 SELECT, from a given list, why the potential exists in a PN junction.
- 2.3.7 SELECT, from a given list, the effect of increasing or decreasing the doping level on the width of the depletion region.
- 2.3.8 SELECT, from a given list, the effect of increasing or decreasing the doping level on the height of the potential.
- 2.3.9 SELECT, from a given list, the factor which affects the total recombination of holes and electrons when a PN junction is formed.
- 2.3.10 DRAW, in the space provided, a forward biased PN junction, showing the source and list the effect of forward bias has on the width of the depletion region.
- 2.3.11 DRAW, in the space provided, the mil-spec symbol for a diode and label the N material, P material, anode, and cathode.

- c. molecule.
- d. atom.

2. Substances made up of atoms of one kind are \_\_\_\_\_
3. Substances made up of different kinds of atoms are called \_\_\_\_\_.
4. An atom is neutral when the number of neutrons equals number of electrons.
- \_\_\_\_\_ a. True
  - \_\_\_\_\_ b. False
5. Group 11 elements have how many valence electrons?
- a. 1
  - b. 2
  - c. 3
  - d. 4
6. Which of the following "valence groups" are insulators?
- a. 4, 5, 6, and 7
  - b. 3, 4, 5, and 6
  - c. 1, 2, and 3
  - d. 5, 6, 7, and 8
7. Covalent bonding in germanium is a method of bonding the atoms share electrons, so that each one will have electrons in its valence shell.
- a. True
  - b. False
8. The "M" shell of an atom could have a maximum of how electrons?
- a. 2
  - b. 6
  - c. 32
  - d. 18

- c. 3
- d. 4

10. A germanium atom contains

- a. four protons.
- b. four valence electrons.
- c. six valence electrons.
- d. only two electron orbits.

11. A normal atom is one which

- a. always has an atomic core with a charge of
- b. always has four valence electrons.
- c. has equal numbers of electrons and protons
- d. shares its electrons with other atoms.

12. When atoms are held together by the sharing of electrons

- a. they form a covalent bond.
- b. they always form a diamond lattice structure
- c. the valence electrons are free to move away
- d. each shared electron leaves a hole.

13. When the temperature of an intrinsic semiconductor

- a. the resistance of the semiconductor increases
- b. the heat decreases the energy of the atoms
- c. holes are created in the conductor band.
- d. the energy of the atom is increased.

14. A hole is the vacancy created when

- a. an electron moves from the conductor band band.
- b. an atomic core moves.
- c. an electron breaks its covalent bond.
- d. a free electron is made to move by an applied

15. The movement of a hole is brought about by the

- a. vacancy being filled by a free electron.
- b. vacancy being filled by a valence electron from a neighboring atom.
- c. movement of the atomic cores.
- d. atomic core changing from 1 +4 to a +5 charge

d. must have only three valence electrons.

The forbidden energy gap in semiconductors

- a. lies just below the valence band.
- b. lies just above the conduction band.
- c. lies between the valence band and the conduction band
- d. is the same as the valence band.

In a P-type semiconductor

- a. the number of holes equals the number of free electrons.
- b. holes are the majority carriers.
- c. the forbidden energy gap is zero.
- d. the impurity is a donor impurity.

In N-type germanium, the

- a. forbidden energy gap is greater than in N-type silicon.
- b. impurity has three valence electrons.
- c. number of holes equals the number of free electrons.
- d. holes are the minority carriers.

The energy required to break a covalent bond in a semiconductor is

- a. equal to 1 eV.
- b. equal to the width of the forbidden gap.
- c. greater in germanium than in silicon.
- d. the same in germanium as in silicon.

Current flow in a P-type semiconductor is

- a. mostly by the movement of free electrons.
- b. by majority carriers only.
- c. by minority carriers only.
- d. mostly by the movement of holes.

In semiconductors, resistivity


- a. is the same as resistance
- b. depends on temperature.
- c. is the same as mobility.
- d. increases as conductivity increases.

- c. charge per carrier.
  - d. temperature and the regularity of the crystal.
24. The change in carrier concentration along the length of a semiconductor is called
- a. diffusion length.
  - b. a concentration gradient.
  - c. recombination rate.
  - d. mobility.
25. When a free electron is recaptured by a hole and a hole, the process is called
- a. recombination.
  - b. diffusion.
  - c. thermal equilibrium.
  - d. lifetime.
26. The movement of charges from an area of high carrier concentration to an area of lower carrier concentration is called
- a. gradient.
  - b. recombination.
  - c. diffusion.
  - d. lifetime.
27. The movement of carriers by an applied voltage is called
- a. drift current.
  - b. diffusion current.
  - c. mobility.
  - d. concentration.
28. Valence electrons are the electrons that take part in forming a covalent bond
- a. true
  - b. false
29. A semiconductor that is electrically neutral has
- a. no free charges.
  - b. no majority carriers.
  - c. equal amounts of positive and negative charges.
  - d. no minority carriers.

- d. is then free to move about.
31. The potential barrier at a PN junction is due to the charges on either side of the junction. These charges are
- majority carriers.
  - minority carriers.
  - both majority and minority carriers.
  - fixed donor and acceptor ions.
32. Holes diffuse from the P region to the N region because
- there is a greater concentration of holes in the P region.
  - they are swept across the junction by the potential difference.
  - the free electrons in the N region attract them.
  - none of these.
33. If the junction current is zero, this means
- the potential barrier has disappeared.
  - the number of holes diffusing from the P region equals the number of electrons diffusing from the N region.
  - there are no carriers crossing the junction.
  - the number of majority carriers crossing the junction equals the number of minority carriers crossing the junction.
34. The junction potential barrier offers opposition to the movement of
- holes in the P region.
  - mobile electrons in the N region.
  - minority carriers in both regions.
  - majority carriers in both regions.
35. Total recombination of all mobile carriers is prevented by
- covalent bonds in the depletion region.
  - mobile carriers in the P-type material.
  - mobile carriers in the N-type material.
  - immobile carriers in the depletion region.

c. positive terminal to P-type material.

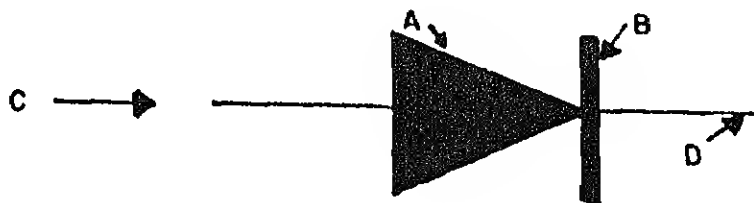37. When forward bias is increased, the potential barrier
- a. lower.
  - b. higher.
  - c. wider.
38. Amount of minority carrier flow depends on
- a. potential of reverse bias.
  - b. potential of forward bias.
  - c. temperature.
  - d. potential barrier height.
39. The amount of reverse bias a PN junction can safely is limited by the
- a. width of the potential barrier.
  - b. amount of power the device can handle.
  - c. type material the device is made of.
  - d. size of the external supply.
40. On the schematic representation of the PN diode below, which element is the cathode?



When PN junctions are formed, what determines the width of depletion region?

- a. type of semiconductor material used
- b. physical size of semiconductor
- c. amount of impurities used in doping
- d. speed at which mobile carriers move

Regarding bias, answer the following (underline the letter the correct choice).

- a. A negative potential connected to the N material of a diode forces the electrons toward/away from the junction.
- b. A negative potential applied to the P material of a diode forces the holes toward/away from the junction.
- c. For majority carrier conduction through a diode, forward reverse bias is applied.
- d. The diode conducts when holes and electrons combine at the junction. True/False



## INTRODUCTION

The purpose of this assignment sheet is to familiarize various aspects of junction transistors. Consideration is given to the characteristics of junction transistors and their operational analysis.

### LESSON TOPIC LEARNING OBJECTIVES

- 3.1.1 SELECT, from a given list, the three basic modes of transistor action.
- 3.1.2 DRAW, in the space provided, the external and internal current paths of a PNP and an NPN transistor.
- 3.1.3 DRAW, in the space provided, a schematic representation of PNP and an NPN transistor, labeling the terminals, voltages and currents with the proper notation.
- 3.1.4 SELECT, from a given list, the correct terminal connections and their relative magnitudes required to properly bias a PNP or an NPN transistor.
- 3.1.5 DEVELOP, equations showing the mathematical relationships between  $I_C$ ,  $I_E$ , and  $I_B$  in a properly biased transistor.
- 3.2.1 DRAW, in the space provided, the three basic transistor circuit configurations.
- 3.2.2 SELECT, from a given list, the characteristic parameters of a common-base amplifier.
- 3.2.3 SELECT, from a given list, the characteristic parameters of a common-collector amplifier.
- 3.2.4 SELECT, from a given list, the characteristic parameters of a common-emitter amplifier.
- 3.2.5 SELECT, from a given list, the main advantages and disadvantages of each of the three configurations.
- 3.2.6 SELECT, from a given list, the effect that temperature has on the reverse current in a PN junction.

input signal.

## QUESTIONS

What are the three basic mechanisms of transistor operation?

\_\_\_\_\_, \_\_\_\_\_, and \_\_\_\_\_.

External current flows in/out the collector and in/out the emitter of an NPN-type transistor.

Majority carriers in an NPN-type transistor are holes/electrons and flow from emitter/collector to emitter/collector.

From a schematic representation of a PNP transistor, how can the emitter element be identified?

What does the notation,  $V_{BE}$  indicate?

For proper bias, what is the polarity relationship of the base to emitter in a PNP transistor?

What is the correct mathematical relationship of transistor currents?

- a.  $I_C = I_E + I_B$
- b.  $I_B = I_C + I_E$
- c.  $I_C = I_C + I_B$
- d.  $I_C = I_E + I_B$

d. input resistance of common-base amplifier.

9. Match notations in "B" to column "A".

Column A

- a. \_\_\_\_\_ B
- b. \_\_\_\_\_ forward bias
- c. \_\_\_\_\_ collector supply
- d. \_\_\_\_\_ most positive element  
of PNP transistors
- e. \_\_\_\_\_ majority carriers  
in NPN transistor
- f. \_\_\_\_\_ minority carriers  
in PNP transistors

Column

- a.  $V_B$
- b.  $V_C$
- c. B
- d. el
- e. ho
- f. co
- g. em
- h.  $I_B$

10. What are the three different circuit configuration transistor can be employed in?

\_\_\_\_\_, \_\_\_\_\_ and \_\_\_\_\_

11. Which circuit configuration is capable of giving h current gain?

12. In the PNP transistor, electrons flow

- a. into the transistor at the emitter and base le
- b. out of the transistor at the emitter and base
- c. into the transistor as the collector and base
- d. out of the transistor at the collector and bas

13. The common-base current transfer ratio is the ratio

a.  $\frac{\Delta I_C}{\Delta I_E}$

b.  $\frac{\Delta I_B}{\Delta I_E}$

c.  $\frac{\Delta I_E}{\Delta I_C}$

d.  $\frac{\Delta I_C}{\Delta I_E}$

- . collector bias supply.
- . collector bias supply less the voltage drop across the load resistor.
- . collector bias supply plus the voltage drop across the load resistor.

When a positive voltage signal is applied to the base of a normally biased NPN common-emitter amplifier the

- . emitter current decreases.
- . collector voltage goes less positive.
- . base current decreases.
- . collector current decreases.

alpha cutoff frequency is where

- . alpha becomes zero.
- . output power is reduced to one-tenth of its original value.
- . alpha becomes .707 its original value.
- . punch-through occurs.

If a transistor is operated at a frequency above the alpha cutoff frequency

- . the transistor will burn out.
- . there will be no output power.
- . the emitter junction must be forward biased.
- . the output current will be reduced.

## INTRODUCTION

The purpose of this assignment sheet is to familiarize you with various aspects of biasing arrangements. Consideration will be given to both the operational analysis and mathematical analysis to determine certain characteristics unique to these circuits.

## LESSON TOPIC LEARNING OBJECTIVES

- 2.9. SELECT, from a given list, what establishes the operating point of a transistor amplifier.
- 2.10. CALCULATE, given a schematic diagram and circuit values, the operating point of a transistor amplifier.
- 2.11. CALCULATE, given a schematic diagram, circuit values, and an input signal, the peak-to-peak amplitude of the output signal of a transistor amplifier.
- 2.12. SELECT, from a given list, the statement that describes the effect of temperature changes on the operating point of a transistor amplifier.
- 2.13. SELECT, from a given list, the definition of  $I_{CQ}$ ,  $I_{CEQ}$ , and  $I_{CQ}$ .
- 2.14. SELECT, from a given list, the need for bias stability.
- 2.15. SELECT, from a given list, the effect that bias stability has on circuit gain ( $A_V$ ).
- 2.16. SELECT, from a given list, how circuit stability is achieved by the addition of an emitter resistor in the common-emitter amplifier.
- 2.17. SELECT, from a given list, the effect on the common-emitter amplifier's gain by the addition of an emitter bypass capacitor.
- 2.18. SELECT, from a given list, the effect on the common-emitter amplifier's stability when a voltage divider is used in the base circuit.
- 2.19. SELECT, from a given list, the effect on the common-emitter amplifier's stability when the collector is returned to the base.

for the stability factor of a given common-emitter amplifier.

2. SELECT, from a given list, the statement that describes  $I_{CQ}$  has a minimum effect on the common-base amplifier.
3. SELECT, from a given list, the effect a continually increasing junction temperature has on an unstabilized common-emitter amplifier.
4. SELECT, from a given list, the statement that describes the common-collector amplifier has inherent temperature stability.

2. What effects are stabilized by the addition of a resistor?
3. By what factor is  $I_{CBO}$  increased in a grounded emitter amplifier?
4. What is the purpose of bias stabilization?
5. What are two factors that will cause an operational amplifier's operating point to shift?
6. What is the need for stabilization when a transistor is replaced?
7. List three methods of increasing the stability of an emitter amplifier.
8. Which amplifier configuration has the best stability?
9. What advantage does a stabilized amplifier have over an unstabilized amplifier?
10. What is the disadvantage of stabilizing an operational amplifier?

## RODUCTION

purpose of this assignment sheet is to familiarize you with various aspects of determining logarithms and their functions in determining the power of various circuits. In this discussion you will find that this power is expressed in decibels. Consideration will be given to the mathematical analysis of the power expressions.

## LEARNING TOPIC LEARNING OBJECTIVES

- 1.1. SELECT, from a given list, the definition of a bel.
- 1.2. SELECT, from a given list, the definition of a decibel.
- 1.3. SELECT, from a given list, the formula which expressed decibels in terms of input and output power.
- 1.4. SELECT, from a given list, the formula which expresses decibels in terms of input and output current.
- 1.5. SOLVE, given the input and output power, for the gain in decibels.
- 1.6. SOLVE, given a power ratio, the decibel equivalent.
- 1.7. SOLVE, given the input power and decibel rating, for the output power.
- 1.8. SOLVE, given a voltage ratio, for the corresponding decibel loss.
- 1.9. SOLVE, given the proper power waveform, the  $F_1$  and  $F_2$  power levels with their proper decibel levels.

## HOMEWORK QUESTIONS

State the definition of a bel.

---



d. 36  $\log_{10}$

3. State the antilogs of the following logarithms.

a. 13. antilog


b. .698 antilog

c. 6.35 antilog


d. 2.0 antilog

4. State the formula for decibels in the terms of input power.

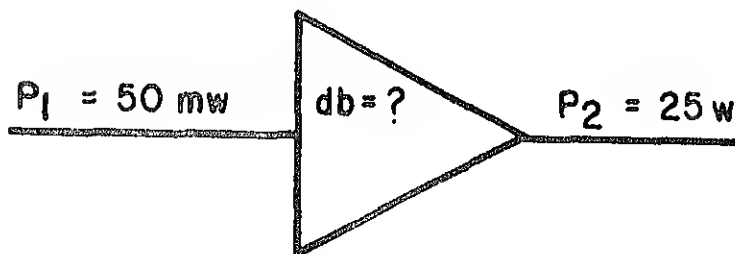5. Solve for the decibel gain of the amplifier below.



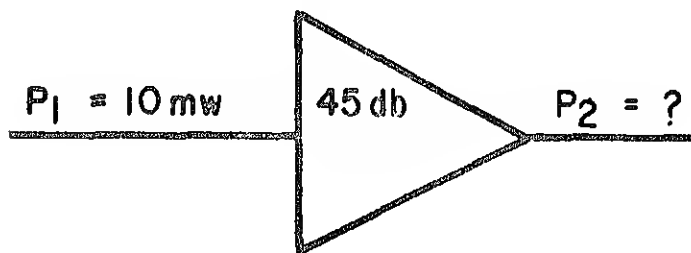6. Solve for the output power of the amplifier below.



$$= 100$$

$$Z_2 = 50$$

State the correct reference (zero) levels for dB, dBm, and dBV.

- a. dB
- b. dBm
- c. dBV

The power at the  $F_1$  point is how many dB below the power at

|    |      |      |      |      |      |      |      |      |      |      |
|----|------|------|------|------|------|------|------|------|------|------|
| 5  | 5990 | 7076 | 7167 | 7243 | 7324 | 7404 | 7482 | 7559 | 7634 | 7709 |
| 6  | 7782 | 7853 | 7924 | 7993 | 8062 | 8129 | 8195 | 8261 | 8325 | 8388 |
| 7  | 8451 | 8513 | 8573 | 8633 | 8692 | 8751 | 8808 | 8865 | 8921 | 8976 |
| 8  | 9031 | 9085 | 9138 | 9191 | 9243 | 9294 | 9345 | 9395 | 9445 | 9494 |
| 9  | 9542 | 9590 | 9638 | 9685 | 9731 | 9777 | 9823 | 9868 | 9912 | 9956 |
| 10 | 1000 | 1043 | 1086 | 1128 | 1170 | 1212 | 1253 | 1294 | 1334 | 1374 |
| 11 | 1414 | 1453 | 1492 | 1531 | 1569 | 1607 | 1645 | 1682 | 1719 | 1755 |
| 12 | 1792 | 1829 | 1864 | 1899 | 1934 | 1969 | 1004 | 1038 | 1072 | 1106 |
| 13 | 1135 | 1173 | 1206 | 1239 | 1271 | 1303 | 1335 | 1367 | 1399 | 1430 |
| 14 | 1444 | 1472 | 1503 | 1533 | 1564 | 1594 | 1624 | 1653 | 1683 | 1712 |
| 15 | 1741 | 1790 | 1818 | 1847 | 1875 | 1903 | 1931 | 1959 | 1987 | 2014 |
| 16 | 2041 | 2068 | 2095 | 2122 | 2148 | 2175 | 2201 | 2227 | 2253 | 2279 |
| 17 | 2304 | 2330 | 2355 | 2380 | 2405 | 2430 | 2455 | 2480 | 2504 | 2529 |
| 18 | 2553 | 2577 | 2601 | 2625 | 2648 | 2672 | 2695 | 2718 | 2742 | 2765 |
| 19 | 2788 | 2810 | 2833 | 2856 | 2878 | 2900 | 2923 | 2945 | 2967 | 2989 |
| 20 | 3010 | 3032 | 3054 | 3075 | 3096 | 3118 | 3139 | 3160 | 3181 | 3201 |
| 21 | 3222 | 3243 | 3263 | 3284 | 3304 | 3324 | 3345 | 3365 | 3385 | 3404 |
| 22 | 3424 | 3444 | 3464 | 3483 | 3502 | 3522 | 3541 | 3560 | 3579 | 3598 |
| 23 | 3617 | 3636 | 3655 | 3674 | 3692 | 3711 | 3729 | 3747 | 3766 | 3784 |
| 24 | 3802 | 3820 | 3838 | 3856 | 3874 | 3892 | 3909 | 3927 | 3945 | 3962 |
| 25 | 3979 | 3997 | 4014 | 4031 | 4048 | 4065 | 4082 | 4099 | 4115 | 4132 |
| 26 | 4150 | 4166 | 4183 | 4200 | 4216 | 4232 | 4249 | 4265 | 4281 | 4297 |
| 27 | 4314 | 4330 | 4346 | 4362 | 4378 | 4393 | 4409 | 4425 | 4440 | 4455 |
| 28 | 4472 | 4487 | 4502 | 4518 | 4533 | 4548 | 4564 | 4579 | 4594 | 4609 |
| 29 | 4624 | 4639 | 4654 | 4669 | 4683 | 4698 | 4713 | 4728 | 4742 | 4757 |
| 30 | 4771 | 4786 | 4800 | 4814 | 4829 | 4843 | 4857 | 4871 | 4886 | 4900 |
| 31 | 4914 | 4928 | 4942 | 4955 | 4969 | 4983 | 4997 | 5011 | 5024 | 5038 |
| 32 | 5051 | 5065 | 5079 | 5092 | 5105 | 5119 | 5132 | 5145 | 5159 | 5172 |
| 33 | 5185 | 5198 | 5211 | 5224 | 5237 | 5250 | 5263 | 5276 | 5289 | 5302 |
| 34 | 5315 | 5328 | 5340 | 5353 | 5366 | 5378 | 5391 | 5403 | 5416 | 5428 |
| 35 | 5441 | 5453 | 5465 | 5478 | 5490 | 5502 | 5514 | 5527 | 5539 | 5551 |
| 36 | 5563 | 5575 | 5587 | 5599 | 5611 | 5623 | 5635 | 5647 | 5658 | 5670 |
| 37 | 5682 | 5694 | 5705 | 5717 | 5729 | 5740 | 5752 | 5763 | 5775 | 5786 |
| 38 | 5798 | 5809 | 5821 | 5832 | 5843 | 5855 | 5866 | 5877 | 5888 | 5899 |
| 39 | 5911 | 5922 | 5933 | 5944 | 5955 | 5966 | 5977 | 5988 | 5999 | 6010 |
| 40 | 6021 | 6031 | 6042 | 6053 | 6064 | 6075 | 6085 | 6096 | 6107 | 6117 |
| 41 | 6128 | 6138 | 6149 | 6160 | 6170 | 6180 | 6191 | 6201 | 6212 | 6222 |
| 42 | 6232 | 6243 | 6253 | 6263 | 6274 | 6284 | 6294 | 6304 | 6314 | 6324 |
| 43 | 6335 | 6345 | 6355 | 6365 | 6375 | 6385 | 6395 | 6405 | 6415 | 6425 |
| 44 | 6435 | 6444 | 6454 | 6464 | 6474 | 6484 | 6493 | 6503 | 6513 | 6523 |
| 45 | 6532 | 6542 | 6551 | 6561 | 6571 | 6580 | 6590 | 6599 | 6609 | 6618 |
| 46 | 6628 | 6637 | 6646 | 6656 | 6665 | 6675 | 6684 | 6693 | 6702 | 6711 |
| 47 | 6721 | 6730 | 6739 | 6749 | 6758 | 6767 | 6776 | 6785 | 6794 | 6803 |
| 48 | 6812 | 6821 | 6830 | 6839 | 6848 | 6857 | 6865 | 6875 | 6884 | 6893 |
| 49 | 6902 | 6911 | 6920 | 6929 | 6937 | 6946 | 6955 | 6964 | 6972 | 6981 |
| 50 | 6990 | 6999 | 7007 | 7016 | 7024 | 7033 | 7042 | 7050 | 7059 | 7067 |
| 1  | 0    | 1    | 2    | 3    | 4    | 5    | 6    | 7    | 8    | 9    |

## COMMON LOGARITHMS

| A  | 0    | 1    | 2    | 3    | 4    | 5    | 6    | 7    | 8    | 9    |
|----|------|------|------|------|------|------|------|------|------|------|
| 50 | 7070 | 7080 | 7090 | 7100 | 7110 | 7120 | 7130 | 7140 | 7150 | 7160 |
| 51 | 7071 | 7081 | 7091 | 7101 | 7111 | 7121 | 7131 | 7141 | 7151 | 7161 |
| 52 | 7072 | 7082 | 7092 | 7102 | 7112 | 7122 | 7132 | 7142 | 7152 | 7162 |
| 53 | 7073 | 7083 | 7093 | 7103 | 7113 | 7123 | 7133 | 7143 | 7153 | 7163 |
| 54 | 7074 | 7084 | 7094 | 7104 | 7114 | 7124 | 7134 | 7144 | 7154 | 7164 |
| 55 | 7075 | 7085 | 7095 | 7105 | 7115 | 7125 | 7135 | 7145 | 7155 | 7165 |
| 56 | 7076 | 7086 | 7096 | 7106 | 7116 | 7126 | 7136 | 7146 | 7156 | 7166 |
| 57 | 7077 | 7087 | 7097 | 7107 | 7117 | 7127 | 7137 | 7147 | 7157 | 7167 |
| 58 | 7078 | 7088 | 7098 | 7108 | 7118 | 7128 | 7138 | 7148 | 7158 | 7168 |
| 59 | 7079 | 7089 | 7099 | 7109 | 7119 | 7129 | 7139 | 7149 | 7159 | 7169 |
| 60 | 7080 | 7090 | 7100 | 7110 | 7120 | 7130 | 7140 | 7150 | 7160 | 7170 |
| 61 | 7081 | 7091 | 7101 | 7111 | 7121 | 7131 | 7141 | 7151 | 7161 | 7171 |
| 62 | 7082 | 7092 | 7102 | 7112 | 7122 | 7132 | 7142 | 7152 | 7162 | 7172 |
| 63 | 7083 | 7093 | 7103 | 7113 | 7123 | 7133 | 7143 | 7153 | 7163 | 7173 |
| 64 | 7084 | 7094 | 7104 | 7114 | 7124 | 7134 | 7144 | 7154 | 7164 | 7174 |
| 65 | 7085 | 7095 | 7105 | 7115 | 7125 | 7135 | 7145 | 7155 | 7165 | 7175 |
| 66 | 7086 | 7096 | 7106 | 7116 | 7126 | 7136 | 7146 | 7156 | 7166 | 7176 |
| 67 | 7087 | 7097 | 7107 | 7117 | 7127 | 7137 | 7147 | 7157 | 7167 | 7177 |
| 68 | 7088 | 7098 | 7108 | 7118 | 7128 | 7138 | 7148 | 7158 | 7168 | 7178 |
| 69 | 7089 | 7099 | 7109 | 7119 | 7129 | 7139 | 7149 | 7159 | 7169 | 7179 |
| 70 | 7090 | 7100 | 7110 | 7120 | 7130 | 7140 | 7150 | 7160 | 7170 | 7180 |
| 71 | 7091 | 7101 | 7111 | 7121 | 7131 | 7141 | 7151 | 7161 | 7171 | 7181 |
| 72 | 7092 | 7102 | 7112 | 7122 | 7132 | 7142 | 7152 | 7162 | 7172 | 7182 |
| 73 | 7093 | 7103 | 7113 | 7123 | 7133 | 7143 | 7153 | 7163 | 7173 | 7183 |
| 74 | 7094 | 7104 | 7114 | 7124 | 7134 | 7144 | 7154 | 7164 | 7174 | 7184 |
| 75 | 7095 | 7105 | 7115 | 7125 | 7135 | 7145 | 7155 | 7165 | 7175 | 7185 |
| 76 | 7096 | 7106 | 7116 | 7126 | 7136 | 7146 | 7156 | 7166 | 7176 | 7186 |
| 77 | 7097 | 7107 | 7117 | 7127 | 7137 | 7147 | 7157 | 7167 | 7177 | 7187 |
| 78 | 7098 | 7108 | 7118 | 7128 | 7138 | 7148 | 7158 | 7168 | 7178 | 7188 |
| 79 | 7099 | 7109 | 7119 | 7129 | 7139 | 7149 | 7159 | 7169 | 7179 | 7189 |
| 80 | 7100 | 7110 | 7120 | 7130 | 7140 | 7150 | 7160 | 7170 | 7180 | 7190 |
| 81 | 7101 | 7111 | 7121 | 7131 | 7141 | 7151 | 7161 | 7171 | 7181 | 7191 |
| 82 | 7102 | 7112 | 7122 | 7132 | 7142 | 7152 | 7162 | 7172 | 7182 | 7192 |
| 83 | 7103 | 7113 | 7123 | 7133 | 7143 | 7153 | 7163 | 7173 | 7183 | 7193 |
| 84 | 7104 | 7114 | 7124 | 7134 | 7144 | 7154 | 7164 | 7174 | 7184 | 7194 |
| 85 | 7105 | 7115 | 7125 | 7135 | 7145 | 7155 | 7165 | 7175 | 7185 | 7195 |
| 86 | 7106 | 7116 | 7126 | 7136 | 7146 | 7156 | 7166 | 7176 | 7186 | 7196 |
| 87 | 7107 | 7117 | 7127 | 7137 | 7147 | 7157 | 7167 | 7177 | 7187 | 7197 |
| 88 | 7108 | 7118 | 7128 | 7138 | 7148 | 7158 | 7168 | 7178 | 7188 | 71   |



## INTRODUCTION

The purpose of this assignment is to familiarize you with the various types and uses of feedback. Consideration will be given to both operational and mathematical analysis of the circuits.

## LESSON TOPIC LEARNING OBJECTIVES

- 3.2.25. SELECT, from a given list, the characteristics of a voltage feedback loop amplifier.
- 3.2.26. SELECT, from a given list, the purpose of a closed-loop amplifier system.
- 3.2.27. SELECT, from a given list, the definitions for  $e_{in}$ ,  $A_f$ , and  $e'_{out}$ .
- 3.2.28. SELECT, from a given list, the definition of regenerative feedback.
- 3.2.29. SELECT, from a given list, the definition of degenerative feedback.
- 3.2.30. SELECT, from a given list, the advantages of a closed-loop feedback system over an open-loop system.
- 3.2.31. CALCULATE, given a transistor amplifier circuit with component values, input signal voltages, and feedback gain,  $e_{in}$ ,  $A_f$ , and  $e'_{out}$ .
- 3.2.32. SELECT, from a given list, the effect that degenerative or regenerative feedback has on the input signal.
- 3.2.33. SELECT, from a given list, the definition of feedback.
- 3.2.34. CALCULATE, given a block diagram of the closed-loop amplifier system with specific values, for the value of  $e'_{out}$ ,  $e_{in}$ ,  $A_f$ , and  $e$ .
- 3.2.35. IDENTIFY, given a schematic diagram of a multistage transistor amplifier using feedback, for the class and type of the feedback used.

1. In a negative feedback system, the phase relationship between the feedback voltage and the input voltage at mid-frequencies would be
- ☐ a. zero.
  - ☐ b.  $90^\circ$ .
  - ☐ c.  $180^\circ$ .
  - ☐ d.  $270^\circ$ .
2. In an amplifier, the effect on stage gain caused by negative voltage feedback is
- ☐ a. increased but constant gain over a wider range of frequencies.
  - ☐ b. decreased but constant gain over a narrower range of frequencies.
  - ☐ c. decreased but constant gain over a wider range of frequencies.
  - ☐ d. increased but variable gain over a narrower range of frequencies.
3. What is the meaning of the expression " $\beta_{out}$ " as used in voltage feedback?
- ☐ a. A fraction of the output voltage used for feedback.
  - ☐ b. The portion of the voltage to be ignored.
  - ☐ c. The part of the output voltage appearing at the collector.
  - ☐ d. The equivalent of the base voltage.
4. Which position of the switch shown in figure 1 would provide degenerative voltage feedback in the circuit?
- ☐ a. A
  - ☐ b. B
  - ☐ c. Both A and B
  - ☐ d. Neither
  - ☐ e. C
5. Why is the degenerative feedback loop normally limited to less than two or three stages of amplification?
- ☐ a. Excessive gain reduction.
  - ☐ b. Possibility of circuit oscillations.
  - ☐ c. Insufficient amplitude of feedback voltage.
  - ☐ d. Excessive reduction in maximum power output (see figure 1).

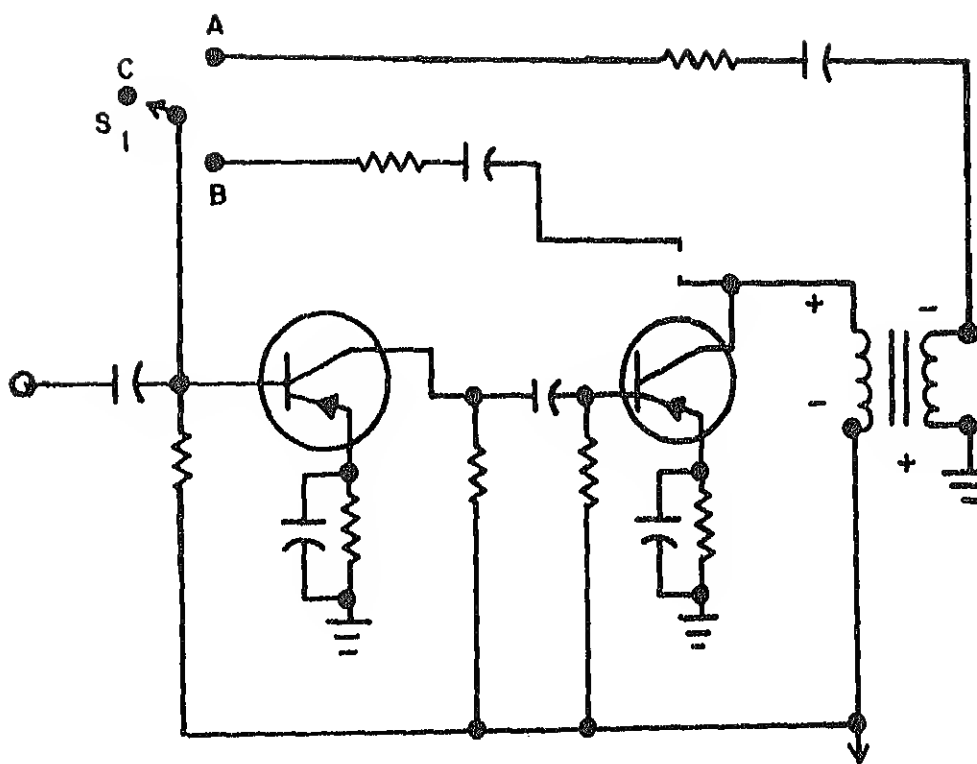


Figure 1



- \_\_\_ d.  $e_{fb}$  is equal to  $R_E \times \Delta I_E$ .
- \_\_\_ e. The type of feedback is voltage feedback.

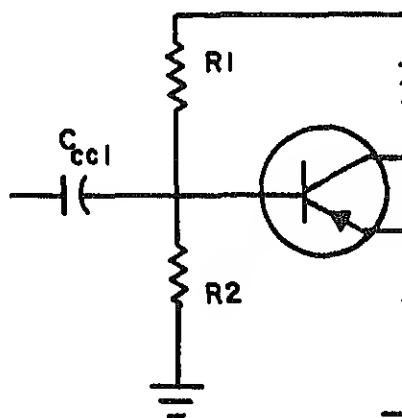


Figure 2

7. Using figure 3, select the correct statements.

- \_\_\_ a. The type of feedback is a-c voltage and a-
- \_\_\_ b. The type of feedback is a-c voltage.
- \_\_\_ c. Beta is the ratio of  $R_i$  to  $R_f + R_i$ .
- \_\_\_ d. Beta is the ratio of  $R_i$  to  $R_f + R_E$ .
- \_\_\_ e.  $C_E$  is to prevent regeneration.


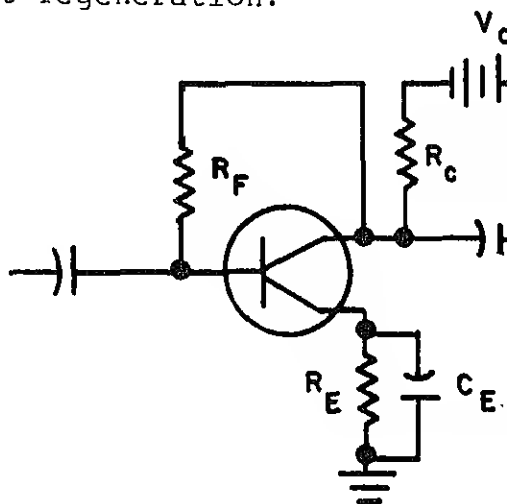


Figure 3

8. In figure 3, if  $C_E$  opens, select the correct statements.

- ☐ a.  $f_2$  increases.
- ☐ b. Output signal increases.
- ☐ c. Degenerative feedback increases.
- ☐ d. Bandwidth decreases.
- ☐ e. Regeneration increases.
- ☐ f. Input resistance increases.
- ☐ g. Output resistance decreases.

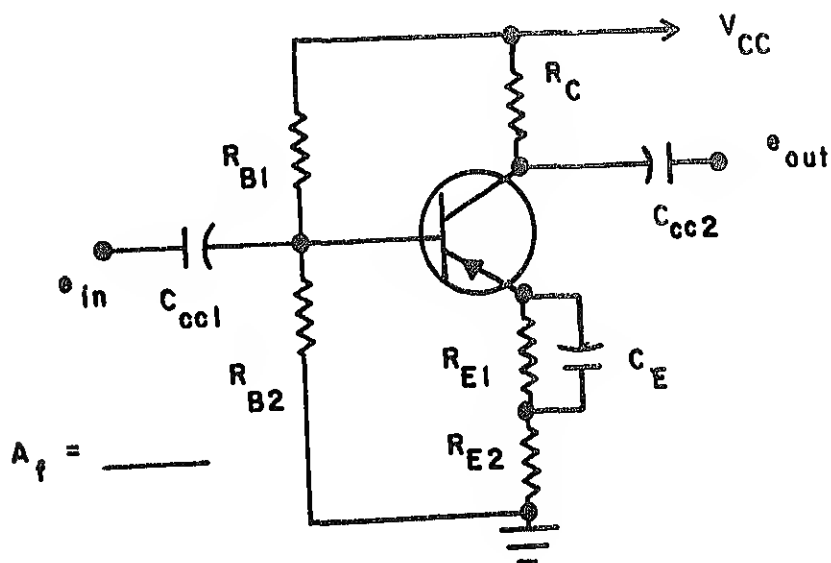9. Using figure 4, compute the gain of the stage with feedback applied.



Given:

$$R_C = 1k \text{ ohms.}$$

$$e_{in} = 2.5.mV$$

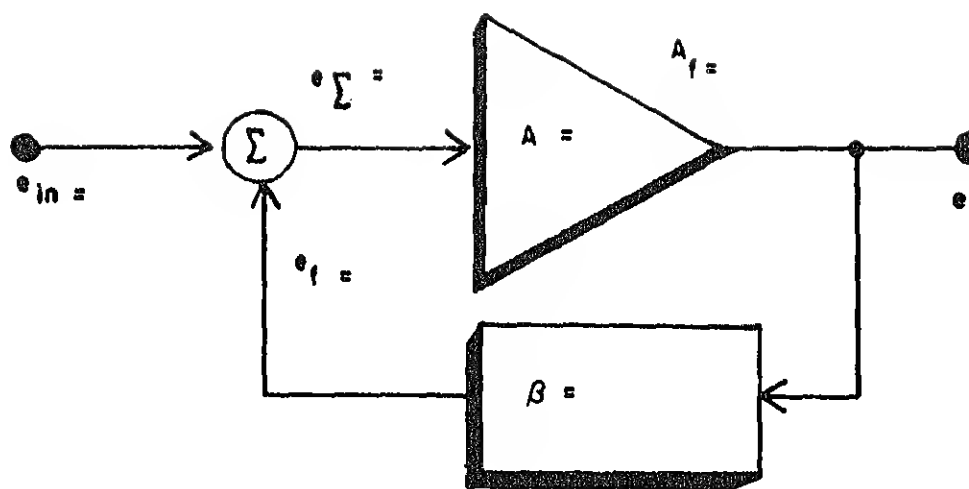


FIGURE 5

One stage of amplification is seldom enough to raise the amplitude of a signal to the required level. The methods of coupling used in a multistage amplifier depends upon many variables. Each method of coupling has its advantages and disadvantages. One method that you will need to concern ourselves with is the direct-coupled multistage amplifier. This assignment sheet is also a self-check to test your understanding of operational amplifiers and their uses. It is essential for technicians have a working knowledge of direct coupling and its characteristics and operation of the op-amp.

## LESSON TOPIC LEARNING OBJECTIVES

- 2.36. SELECT, from a given list, the reason why coupling capacitors are not used in direct-coupled amplifiers.
- 2.37. SELECT, from a given list, the major advantages of direct coupling.
- 2.38. SELECT, from a given list, the reason why component values for direct coupling must be carefully chosen.
- 2.39. SELECT, from a given list, the reason for using common-emitter connected transistors.
- 2.40. SELECT, from a given list, the purpose of the balanced differential amplifier.
- 2.41. SELECT, from a given list, the desirable characteristics of a balanced differential amplifier.
- 2.42. SELECT, from a given list, the definition of an operational amplifier.
- 2.43. SOLVE, for the output voltage of an op-amp when given the input voltage, feedback impedance, and input impedance.
- 2.44. SELECT, the standard symbol for a differential amplifier.
- 2.45. SELECT, the correct statement that describes the operation of a differential amplifier.
- 2.46. COMPUTE, the output of a differential amplifier when given a schematic diagram, component values, and input voltages.

- b. Frequency response
- c. Complicated circuitry
- d. Expensive to construct

2. Direct-coupled amplifiers are normally used when
- a. large signal inputs are used
  - b. high frequencies are applied to the circuit
  - c. when a narrow bandwidth is required
  - d. amplification of direct current (zero frequency) required
3. What type of compound connected circuit allows almost current gain?
- a. Complementary symmetry
  - b. Common-emitter configuration
  - c. Common-base configuration
  - d. Common-collector configuration
4. Write the definition of an operational amplifier.

---

---

5. Describe the relative amplitude of the voltage deviation at the summation junction of an op-amp.

---

---

6. Describe the output of a summing amp.

---

feedback paths.

Calculate the output voltage of a differential amplifier if the input resistors are 10 kohms, the feedback is 5 kohms, and the input voltages are both 2Vd-c.

\_\_\_\_\_ Vd-c

What happens to the gain of a basic op-amp if the input resistance is increased in value?

Describe the open-loop gain and the closed-loop gain in a basic op-amp.

Open-loop gain \_\_\_\_\_

Closed-loop gain \_\_\_\_\_

State several applications of op-amps. \_\_\_\_\_

If the input resistor and feedback resistor are both equal to 1 megohm, what is the gain of the circuit?

If  $R_f$  is increased, what happens to gain of the stage?

Find  $E_o$  in the circuit below.

Where:

$R_{in} = 1.5 \text{ Megohm}$

$R_f = 1 \text{ Megohm}$

$E_{in} = 4.5 \text{ V}$



## DUCTION

age of amplification is seldom enough to raise the amplitude to the required level. The methods of coupling used in each stage amplifier depends upon many variables. Each method has its advantages and disadvantages. The method that we need to concern ourselves with is transformer coupling. It is essential that we as technicians have a working knowledge of transformer coupling.

## ON TOPIC LEARNING OBJECTIVES

47. SELECT, from a given list, the major advantage of transformer coupling.
48. SELECT, from a given list, the major disadvantage of transformer coupling.
49. SELECT, from a given list, the losses incurred in transformer circuits.
50. SELECT, from a given list provided, the definitions of core currents, hysteresis losses, copper losses, and flux leakage.
51. CALCULATE, given a transformer and specific values,  $E_x$ ,  $I_p$ ,  $I_s$ ,  $Z_p$ , and  $Z_s$ .
52. SELECT, from a given list, the characteristics which determine the high and low frequency response of a transformer.



- c. Poor power gain
  - d. Large size
2. An iron-core transformer is connected to a 115 volt source and draws 38.6 mA of current. The output voltage is 230 volts and the secondary current is 18.9 mA. The transformer's efficiency is
- a. 10.2%.
  - b. 50%.
  - c. 95%.
  - d. 98%.
3. A transformer loss that is NOT heat, but which decreases transformer efficiency is
- a. eddy currents.
  - b. copper loss.
  - c. flux leakage.
4. Which of the following helps reduce eddy currents in a transformer core?
- a. Use of high-permeability, low-retentivity cores
  - b. Use of laminated or powdered-iron cores
  - c. Use of shell or core type transformers
  - d. Use of low-reluctance paths for flux
5. If 386 volts is measured across the secondary of a transformer whose turns ratio is 1:5.15, how much voltage is applied to the primary winding?
- a. 51.5 volts
  - b. 75.0 volts
  - c. 19.9 volts
  - d. 76.5 volts
6. The turns ratio is required to match a 10 ohm speaker to a 400 ohm source impedance is
- a. 1:1.
  - b. 60:1.
  - c. 6:1.
  - d. 38:1.

## INTRODUCTION

The purpose of this assignment sheet is to familiarize you with various types of special transistor devices that you as an electronic technician will encounter. Consideration will be given to the operational characteristics as well as the internal structure of the devices studied.

### LESSON TOPIC LEARNING OBJECTIVES

- 3.2.53. SELECT, from a given list, the advantages of a JFET compared to a bipolar device.
- 3.2.54. IDENTIFY, given the mil-spec symbol for a JFET, the gate, drain and source.
- 3.2.55. SELECT, from a list of statements, the effect of gate area and drain current for an input signal polarity on N- or P-channel JFET.
- 3.2.56. LABEL, given the mil-spec symbol for an N-channel or P-channel JFET, the biasing polarities required for gate, drain, and the source for normal operation.
- 3.2.57. LABEL, given the mil-spec symbol for an N- or P-channel enhancement MOSFET, for the bias polarities required for gate, drain, and source for normal operation.
- 3.2.58. SELECT, from a list of statements, for the effect of channel area and drain current for a given input signal polarity on the N- or P-channel enhancement MOSFET.
- 3.2.59. LABEL, given the mil-spec symbol for an N- or P-channel depletion MOSFET, for the bias polarities required for gate, drain, and source for normal operation.
- 3.2.60. SELECT, from a list of statements, for the effect of channel area and drain current for a given input signal polarity on an N- or P-channel depletion MOSFET.
- 3.2.61. SELECT, from a given list, the difference in characteristics for a zener and a normal PN junction diode.
- 3.2.62. SELECT, from a given list, the characteristics that determine the breakdown voltage on a zener diode.

- SCR.
6. LABEL, on a given diagram, the anode, cathode, and the gate of an SCR with the polarities needed for proper operation.
  7. SELECT, from a given list of statements, the one which best describes the difference between a Silicon Controlled Rectifier and a Shockley diode.
  8. LABEL, on a given diagram,  $B_1$ ,  $B_2$  the emitter, and the proper polarities for normal operation of the Unijunction Transistor.
  9. CALCULATE, given a diagram of a UJT with interbase voltage and intrinsic standoff ratio, for the firing potential.

## QUESTIONS

How does the JFET differ from the bipolar transistor in that it

- 1. has unipolar majority carriers.
- 2. is a voltage controlled device.
- 3. resembles a pentode vacuum tube.
- 4. utilizes a forward-biased PN junction for control of unipolar carriers.

What polarities of bias voltage would be applied to a JFET's gate and drain for an N-channel? A P-channel?

As the gate voltage is increased in a JFET, what happens to the depletion region and drain current?

5. List some of the advantages of the JFET.
6. What polarities of bias voltage would be applied to an enhancement MOSFET's gate and drain for an N-channel? A P-channel?
7. What is the major difference between a JFET and an enhancement MOSFET in respect to biasing?
8. The zener diode operates on
  - a. majority carriers and is normally forward biased.
  - b. majority carriers and is normally reverse biased.
  - c. minority carriers and is normally forward biased.
  - d. minority carriers and is normally reverse biased.
9. The impedance of a PNPN diode prior to breakdown is
  - a. low because of charge multiplication.
  - b. high because of an internal reverse-biased junction.
  - c. low because of two forward-biased junctions.
  - d. high because of a small value of minority current.
10. In the basic SCR, the gate can/cannot initiate turn-on.
11. In the SCR, after breakover,
  - a. current flow is equal to  $I_H$  and is constant.
  - b. load current is limited by load resistance.
  - c. load current is equal to the gate current.
  - d. load voltage is equal to the voltage across the SCR.
  - e. the SCR cannot be commutated.



The purpose of this assignment sheet is to familiarize students with various aspects of vacuum tube fundamentals. Consideration is given to both the operational characteristics as well as the mathematical analysis of the circuits.

#### LESSON TOPIC LEARNING OBJECTIVES


- 4.1.1. SELECT, from the list provided, the four types of vacuum tube emission.
- 4.1.2. MATCH, from the list provided, the component of a vacuum tube with their functions.
- 4.1.3. SELECT, from the list provided, the definition of "Full Charge."
- 4.1.4. SELECT, from the list provided, for the output of a given vacuum tube diode rectifier circuit.

- a. The plate
  - b. The filament
  - c. The control grid
  - d. The cathode
2. Which tube element is normally used for heat dissipation?
- a. The filaments
  - b. The envelope
  - c. The plate
  - d. The cathode
3. Which type of emission is the most commonly used?
- a. Cold cathode
  - b. Thermionic
  - c. Secondary
  - d. Photoelectric
4. From the list below, select the correct statement(s) about the SPACE CHARGE.
- a. It is a space between two or more charged particles.
  - b. It is a cloud of electrons.
  - c. It is never depleted to zero.
  - d. It exists in vacuum tubes which use thermal emission.
  - e. It limits the number of electrons being emitted from the cathode.
  - f. It may also be known as the VIRTUAL CATHODE.
  - g. It is a cloud of holes.
5. What are the two methods of heating the cathode?
- a. \_\_\_\_\_ and \_\_\_\_\_.
6. Define plate saturation.

---

---

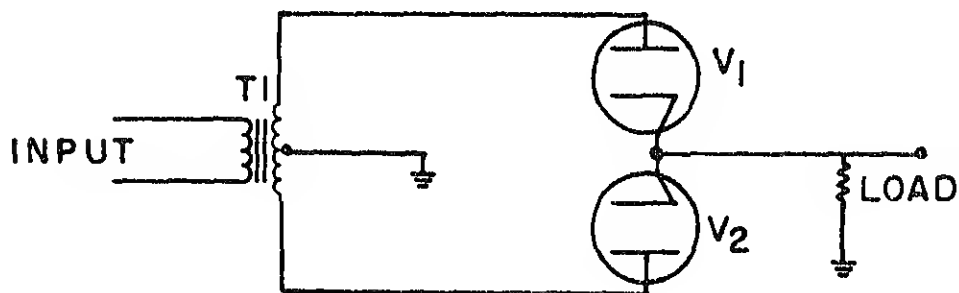- c. Both the positive and negative half cycle.  
d. None of the above-







The purpose of this assignment sheet is to familiarize various aspects of triode vacuum tubes. Consideration to both the operational analysis and the mathematical as well as certain characteristics unique to triode vacuum

#### LESSON TOPIC LEARNING OBJECTIVES

- 4.2.1 SELECT, from a given list, the statement which the placement of the control grid in a triode v
- 4.2.2 SELECT, from a given list, the statement which the effect on plate current for given changes in voltage.
- 4.2.3 SELECT, from a given list, the definition for  $r_p$ .
- 4.2.4 SELECT, given the schematic diagram of a triode circuit, component values, and an  $E_b - I_b$  graph line, the correct values of plate current for a grid voltage.
- 4.2.5 DETERMINE, given an  $E_b - I_b$  graph with a load line, change in plate current for given changes in grid voltage.
- 4.2.6 MATCH, given a list of vacuum tube circuit notation with its proper definition.

tetrode.  
pentode.  
triode.  
variable  $\mu$ .

Which electrostatic field, in a triode, has the greatest effect on tube current? The field between the

screen grid and plate.  
control grid and plate.  
control grid and cathode.  
cathode and filament.

Which plate voltage is designated by the circuit notation

$E_{bb}$   
 $E_b$   
 $e_b$   
 $e_p$

Which tube element voltages are measured with respect to the

plate.  
control grid.  
cathode.  
supply voltage.

Select, from the list below, the definition of bias.

The a-c difference of potential applied to the control grid.  
The d-c difference of potential between the control grid and plate.  
The d-c difference of potential between the control grid and the cathode.  
The d-c difference of potential between the cathode and the plate.

Which term  $\mu$  ( $\mu$ ) is used to express

transconductance.  
a-c plate resistance.  
d-c plate resistance.  
amplification factor.

- b. between grid voltage and grid current.
  - c. between grid voltage and plate current.
  - d. plate voltage and grid current.
8. Which statement is true relative to the position of the load resistor in a triode amplifier circuit? It is connected
- a. parallel with the a-c plate resistance of the tube.
  - b. series with the a-c plate resistance of the tube.
  - c. parallel with the plate supply voltage.
  - d. series with the grid resistor.
9. What is the relationship of the three voltages found in the circuit of a triode amplifier?
- a.  $E_b = E_{R_L} + E_{bb}$
  - b.  $E_{R_L} = E_b - E_{bb}$
  - c.  $E_{bb} = E_b + E_{R_L}$
  - d.  $E_b = E_{R_L} - E_{bb}$
10. What two values must be known to construct a load line?
- a.  $R_L$  and  $E_b$ .
  - b.  $E_{bb}$  and  $E_{R_L}$ .
  - c.  $E_L$  and  $I_b$ .
  - d.  $E_{bb}$  and  $E_{cc}$ .
11. In addition to determining the maximum amplitude of the dynamic transfer curve (DTC) may also be used to determine the operating point of the tube.
- a. True.
  - b. False.

- 0. transconductance.
- 1. voltage gain.
- 1. interelectrode capacitance.

The purpose of this assignment sheet is to familiarize you with various aspects of the multielement vacuum tubes. Consideration is given to the construction, operation and the characteristics of each type of vacuum tube.

#### LESSON TOPIC LEARNING OBJECTIVES

- 2.7. SELECT, from a given list, the major disadvantage of the tetrode vacuum tube.
- 2.8. SELECT, from a given list, the major advantage of the vacuum tube.
- 2.9. SELECT, from a given list, the major advantage of the beam-power tube.
- 2.10. MATCH, given a list of CRT elements and a list of element functions, each element with its function.

#### STUDY QUESTIONS

Select, from the list below, the correct statements concerning the tetrode.

- a. The screen grid is normally operated at a positive dc potential.
- b. The suppressor grid is normally operated at cathode potential.
- c. The tetrode has four elements.
- d. The tetrode has less interelectrode capacitance than the triode.
- e. The tetrode has less interelectrode capacitance than the pentode.
- f. The tetrode has a higher value of a-c plate resistance than the triode.
- g. The tetrode is capable of a larger voltage gain than the triode.
- h. The tetrode has a wide operating range.

3. Which of the items listed below is not an element of the pentode.
- a. Control grid.
  - b. Buncher grid.
  - c. Suppressor grid.
  - d. Screen grid.
4. Concerning the pentode, which of the items listed below
- a. The suppressor grid reduces secondary emission
  - b. The pentode has a lower value of interelectrode capacitance
  - c. The pentode is capable of a higher voltage gain than a diode or triode
  - d. The pentode has a wider operating range than the triode
5. Concerning the beam-power tube, the virtual suppressor is located by the
- a. cathode.
  - b. control grid.
  - c. plate.
  - d. beam-forming plates.
6. Which item(s) listed below are not elements of a CRT?
- a. Accelerating anode.
  - b. Buncher grid.
  - c. Phosphor screen.
  - d. Focusing anode.
  - e. Deflection system.
  - f. Suppressor grid.
  - g. Aquadag coating.
7. The electronic lens is used to concentrate the electron beam to light up the phosphor screen.
- a. True
  - b. False

- b. aperture width.
- c. intensity.
- d. none of the above.

9. The aquadag coating is used to

- a. prevent light from entering the back of the CR
- b. focus the electron beam.
- c. prevent secondary emission.
- d. prevent a negative charge from building up on





$$1. \quad X_L = 2\pi fL$$

$$2. \quad X_C = \frac{1}{2\pi fC}$$

#### SERIES ONLY

$$1. \quad Z_O = R$$

$$2. \quad E_{XL} \text{ or } E_{XC} = Q E_A$$

#### PARALLEL ONLY

$$1. \quad Z_T = \frac{Z_1 Z_2}{Z_1 + Z_2}$$

$$2. \quad Z_O = \frac{E_A}{I_{line}}$$

$$3. \quad Z_O = QX_L$$

$$4. \quad Z_O = Q^2 R$$

$$5. \quad Z_O = \frac{(X_L)^2}{R}$$

$$6. \quad Z_O = \frac{L}{RC}$$

$$7. \quad I_{tank} = Q I_{line}$$

$$8. \quad P_t = P_a \cos \theta$$

$$9. \quad P_f = \frac{P_t}{P_a} = \cos \theta$$

$$1. \quad \beta = \frac{I_C}{I_B}$$

$$2. \quad \beta = \frac{\alpha}{1 - \alpha}$$

$$3. \quad I_{CEO} = I_{CBO}(\beta + 1)$$

$$4. \quad I_C = (\beta)(I_B) + (I_{CBO})$$

#### COMMON BASE AMPLIFIER

$$1. \quad \alpha = \frac{I_C}{I_E}$$

$$2. \quad \alpha = \frac{\beta}{\beta + 1}$$

#### COMMON COLLECTOR AMPLIFIER

$$1. \quad \gamma = \frac{I_E}{I_B}$$

$$2. \quad \gamma = \beta + 1$$

#### BIAS STABILITY

$$1. \quad S = \frac{(R_B + R_E)(\beta + 1)}{R_B + (\beta + 1) R_1}$$

$$2. \quad Q = \frac{X_L}{R}$$

$$3. \quad BW = \frac{F_O}{Q}$$

$$4. \quad BW = \frac{R}{2\pi L}$$

$$5. \quad X_L = X_C = L/C$$

$$6. \quad F_O = \frac{X_L}{2\pi L}$$

### DECIBEL

$$A. \quad dB = 10 \log(10) \frac{P_2}{P_1}$$

$$B. \quad dB = 20 \log(10) \frac{E_2}{E_1} \sqrt{\frac{Z_1}{Z_2}}$$

$$C. \quad dB = 20 \log(10) \frac{I_2}{I_1} \sqrt{\frac{Z_2}{Z_1}}$$

### FEEDBACK AMPLIFIERS

$$A. \quad A_f = \frac{A_v}{1 - \beta A_v}$$

$$B. \quad e_\varepsilon = e_{in} + \beta e'_{out} = e_{in} + e_f$$

$$C. \quad e'_{out} = \frac{A_v e_{in}}{1 - \beta A_v} = e_{in} A_f = e_\varepsilon A_v$$

### OP-AMPS

$$A. \quad E_{out} = (E_{in2} \frac{R_f}{R_{s2}}) + (- E_{in1} \frac{R_f}{R_{s1}})$$

$$B. \quad E_{out} = e_{in} \frac{R_f}{R_s}$$

### TRANSFORMER RELATIONSHIPS

$$A. \quad TR = \frac{N_p}{N_s} = \frac{E_p}{E_s} = \frac{I_s}{I_p} = \sqrt{\frac{Z_p}{Z_s}}$$

$$B. \quad Z_p = (TR)^2 (Z_s)$$

### VACUUM TUBE FUNDAMENTALS

A. D-c Plate Resistance

$$1. \quad R_p = \frac{E_b}{I_b}$$

B. A-c Plate Resistance

$$1. \quad r_p = \frac{\Delta E_b}{\Delta I_b}$$

### TRIODES

A. Amplification Factor

$$1. \quad \mu = \frac{\Delta e_b}{\Delta e_c} = (gm)(r_p)$$

B. Transconductance

$$1. \quad gm = \frac{\Delta i_b}{\Delta e_c} = (\mu)(r_p)$$



